 



Digital Systems - Mahdi Bohloul - CA1 - Report



nmos # (3,4,5)

pmos # (5,6,7)

Hand simulate → Intt → a50, b50 →

 



Two input nand

```
`timescale 1ns/1ns

module TwoINand(input a, b, output w);
    supply1 Vdd;
    supply0 Gnd;
    wire y1;
    pmos #(5,6,7) T1(w, Vdd, a), T2(w, Vdd, b);
    nmos #(3,4,5) T3(y1,Gnd,a), T4(w,y1,b);
endmodule
```




Two input nand testbench

```
`include "TwoInputNand.v"

`timescale 1ns/1ns


 
module TwoINand_TB( );
    reg aa=0,bb=0;
    wire ww;
    TwoINand two_nand(.a(aa), .b(bb), .w(ww));
    initial begin
        #15
        #20 aa=1;
        #30 bb=1;
        #40 aa=0;bb=0;
        #55 aa=1;bb=1;
        #20 $stop;
    end
endmodule
```



②: Tri-state buffer schematic

EN	A	w
0	0	Z
0	1	Z
1	0	1
1	1	0

$$w = EN \cdot A$$

 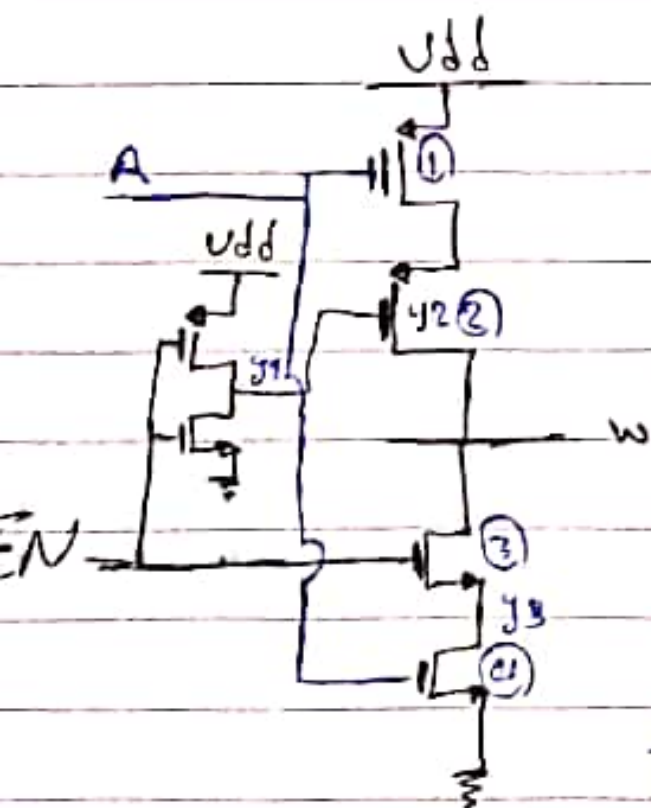

The worst case occurs when EN=1 and A turns from 0 to 1, transistor ① takes T_{ns} for T_{oz} , and transistor ② has output 1 so far, takes T_{ns} .

sam

And two nmos transistors take 8ns to give 0 as output. As a result, we will have

X in $\boxed{14 - 8 = 6 \text{ ns}}$ \rightarrow $\boxed{\text{worst case} = 14 \text{ ns}}$ \rightarrow To 0

To 1 \rightarrow Assuming $A = 1$, E_{in} turns to 1 from 0 \rightarrow inverter delay: $T_{ris} + \text{prop-to-1 delay} = 5$
 $\rightarrow 7 + 5 = 12 \text{ ns}$



Tri-State Buffer

```
`timescale 1ns/1ns
```


```
module TriStateBuffer(input en, a, output w);  
    supply1 Vdd;  
    supply0 Gnd;  
    wire y1, y2, y3;  
    pmos #(5,6,7) T1(y1,Vdd,en), T3(y2,Vdd,a), T4(w,y2,y1);  
    nmos #(3,4,5) T2(y1,Gnd,en), T5(y3,Gnd,a), T6(w,y3,en);  
endmodule
```




Tri-State Buffer testbench

```
`include "TriStateBuffer.v"
`timescale 1ns/1ns

module TriStateBufferTb();
    reg en=0,bb=0;
    wire ww;
    TriStateBuffer tri_state(.en(en), .a(bb), .w(ww));
    initial begin
        #15
        #20 en=1;
        #35 bb=1;
        #50 en=0;bb=0;
        #70 en=1;bb=1;
        #20 $stop;
    end
endmodule
```

 3

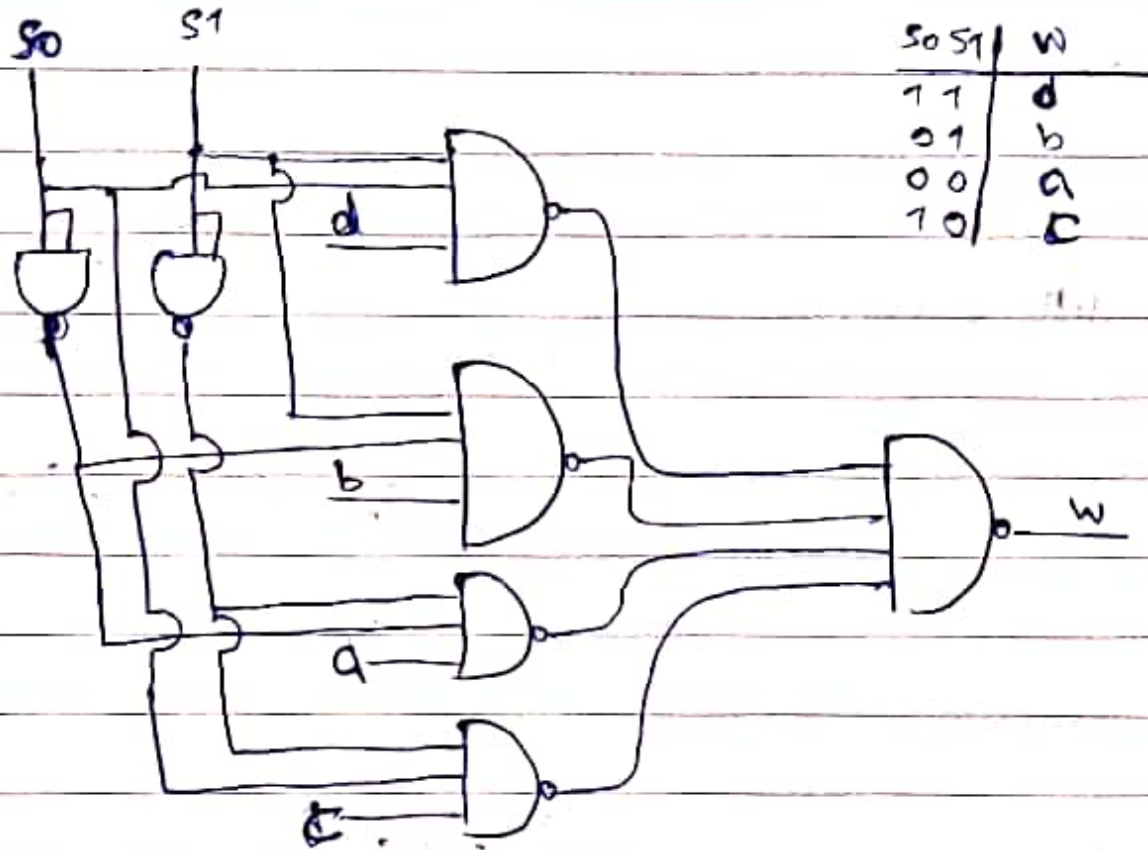

S0	S1	W
1	1	d
0	1	b
0	0	a
1	0	c

delay time for 2 input NAND gate $\rightarrow T_{01}: 1\text{ns}, T_{00}: 8\text{ns}$

" " " 3 input NAND gate $\rightarrow T_{01}: 15\text{ns}, T_{00}: 12\text{ns}$

" " " 4 input NAND gate $\rightarrow T_{01}: 20\text{ns}, T_{00}: 16\text{ns}$



Three input nand

```
`timescale 1ns/1ns
```

```
module ThreeInputNand(input a,b,c, output w);  
    supply1 Vdd;  
    supply1 Gnd;  
  
    wire y1,y2;  
    pmos #(5,6,7) T1(w,Vdd,a), T2(w,Vdd,b), T3(w,Vdd,c);  
    nmos #(3,4,5) T4(w,y2,a), T5(y2,y1,b), T6(y1,Gnd,c);  
endmodule
```



Four input nand

```
`timescale 1ns/1ns
```

```
module FourInputNand(input a,b,c,d, output w);  
    supply1 Vdd;  
    supply1 Gnd;  
  
    wire y1,y2,y3;  
    pmos #(5,6,7) T1(w,Vdd,a), T2(w,Vdd,b), T3(w,Vdd,c), T4(w,Vdd,d);  
    nmos #(3,4,5) T5(w,y3,a), T6(y3,y2,b), T7(y2,y1,c), T8(y1,Gnd,d);  
endmodule
```



Nand 4-To-1 MUX

```
`include "TwoInputNand.v"
`include "ThreeInputNand.v"
`include "FourInputNand.v"

`timescale 1ns/1ns

module NandMUX(input a,b,c,d,s0,s1, output w);
    wire s0_bar, s1_bar;
    wire a_s, b_s, c_s, d_s;
    TwoINand invert_s0(s0,s0,s0_bar);
    TwoINand invert_s1(s1,s1,s1_bar);
    ThreeInputNand select_a(s0_bar, s1_bar, a, a_s);
    ThreeInputNand select_b(s0_bar, s1, b, b_s);
    ThreeInputNand select_c(s0, s1_bar, c, c_s);
    ThreeInputNand select_d(s0, s1, d, d_s);
    FourInputNand result(a_s, b_s, c_s, d_s, w);
endmodule
```




Nand 4-To-1 MUX testbench

```
`include "4To1MUX.v"


`timescale 1ns/1ns

module NandMUXTB( );
    reg aa=0,bb=0,cc=0,dd=0,ss0=1,ss1=1;
    wire ww;
    NandMUX mux(aa,bb,cc,dd,ss0,ss1,ww);

 
    initial begin
        #50
        #50 aa=1; ss0=0; ss1=0;
        #50 bb=1; ss1=1;
        #50 dd=1; ss0=1; ss1=1;
        #50 ss0=0; ss1=1;
        #50 $stop;
    end
endmodule
```



④: Convert 4-To-1 MUX to 3 2-To-1 Mux →

 

 
Now Create a 2-To-1 MUX with Tri-state buffer →



Truth table →


S_0	w
0	a
1	b

 , Now according to question two we know the structure of our Tri-state buffer is as follow:




sa.m

 Now we create the 4-to-1 MUX using this structure →



Now, according to the drawn schematic, we know that the inverters of part (I) neutralize the inverters of Part (II) and there is no change in the output of our circuit.

 If we want \bar{S}_0 or \bar{S}_1 → $X \xrightarrow{V_{DD}} \bar{X}$



Assume $a=1, b=0, c=1, d=0$
 $S_0, S_1=0$

$S_0: 0 \rightarrow 1$ → delay time $\begin{matrix} \text{①} \text{③} 14 \text{ (Tri-state Inverter } T_{00}) + 12 \text{ (Tri-state } \text{⑦} T_{02}) \\ \text{②} \text{④} 12 \text{ (Tri-state } T_{01}) \end{matrix}$
 → 14 ns → X

$S_1: 0 \rightarrow 1$ → In the first 26 ns it looks like S_0 and after that it becomes 1 as input → 14 ns (Tri-state T_{00})

worst case delay → 40 ns : T_{00}

T_{00} → $S_0: 1 \rightarrow 0$ → delay time $\begin{matrix} \text{①} \text{③} 12 \text{ (Tri-state Inverter } T_{01}) + 14 \text{ (Tri-state } T_{00}) \\ \text{②} \text{④} 14 \text{ (Tri-state } T_{00}) \end{matrix}$
 → 12 ns → X

$S_1: 1 \rightarrow 0$ → delay time → 26 ns same as S_0 and after that it becomes 0 as input →

12 ns (Tri-state T_{01}) \rightarrow Worst-case \rightarrow 38 ns $\rightarrow T_{01}$



Tri-State Buffer 4-To-1 MUX

```
`include "TriStateBuffer.v"

`timescale 1ns/1ns

module TriStateMUX(input a,b,c,d,s0,s1, output w);
    supply1 Vdd;
    supply0 Gnd;

    wire s0_inv, s1_inv;
    wire mux1_out, mux2_out;

    TriStateBuffer invert_s0(.en(Vdd), .a(s0), .w(s0_inv));
    TriStateBuffer invert_s1(.en(Vdd), .a(s1), .w(s1_inv));
    TriStateBuffer select_a(.en(s0_inv), .a(a), .w(mux1_out));
    TriStateBuffer select_b(.en(s0), .a(b), .w(mux1_out));
    TriStateBuffer select_c(.en(s0_inv), .a(c), .w(mux2_out));
    TriStateBuffer select_d(.en(s0), .a(d), .w(mux2_out));

    TriStateBuffer select_mux1(.en(s1_inv), .a(mux1_out), .w(w));
    TriStateBuffer select_mux2(.en(s1), .a(mux2_out), .w(w));

endmodule
```




Tri-State Buffer 4-To-1 MUX testbench

```
`include "TriState4To1MUX.v"


`timescale 1ns/1ns

module TriStateMUXTB( );
    reg aa=1,bb=0,cc=1,dd=0,ss0=0,ss1=0;
    wire w;
    TriStateMUX tri_state_mux(aa,bb,cc,dd,ss0,ss1,w);

     initial begin
        #100
        #30 ss0=1;ss1=1;
        #50 bb=0;dd=0;
        #30 ss0=0;
        #30 ss1=0;
        #50 $stop;
    end
endmodule
```



5/4

 

Power Consumption → Because the number of series transistors in NAND-MUX is higher, its power consumption is also higher

	To 0	To 1
NAND-MUX	38 ns	45 ns
Tri-state	40 ns	38 ns



Tri-State buffer MUX vs Nand MUX

```
`include "TriState4To1MUX.v"
`include "4To1MUX.v"

`timescale 1ns/1ns

module TriStateMUXCompareNandMUXTB( );
    reg aa=0,bb=0,cc=0,dd=0,s0=0,s1=0;
    wire ww1,ww2;

    NandMUX nand_mux(aa,bb,cc,dd,s0,s1,ww1);
    TriStateMUX tri_state(aa,bb,cc,dd,s0,s1,ww2);

    initial begin
        #50
        #100 s0=1;s1=1;
        #100 bb=1;dd=1;
        #100 aa=1;cc=1;
        #100 $stop;
    end
endmodule
```